

EE 230 Experiment - 1

NGSpice Familiarization

30th July, 2021



Vinamra Baghel

190010070


1 RC Integrator

PartB1.cir:
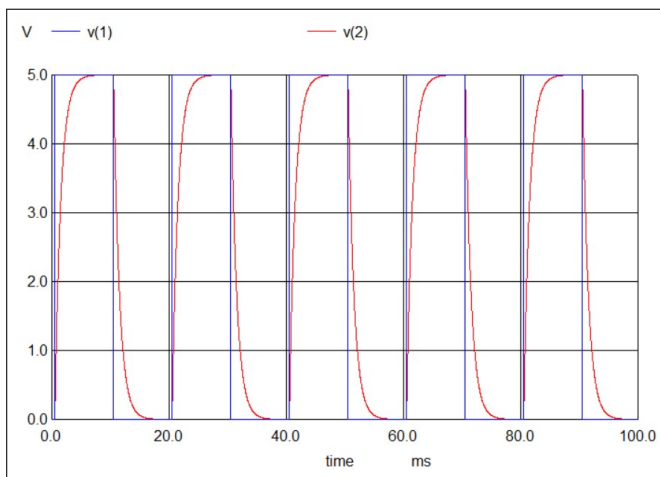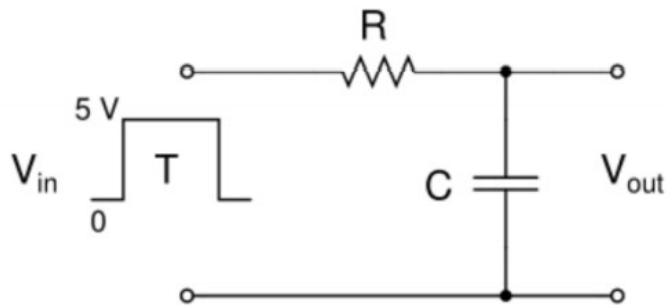
```
1 B1. RC Integrator Vinamra Baghel 190010070
2 * <element-name> <nodes> <value/model>
3 r 1 2 10k
4 c 2 0 0.1u
5 v 1 0 pulse(0 5 0.25m 0 0 0.05m 0.1m)
6 *analysis command
7 .tran 10u 7m
8 .control
9 run
10 plot v(2) v(1)
11 .endc
12 .end
```



(a) $T = 10\tau$

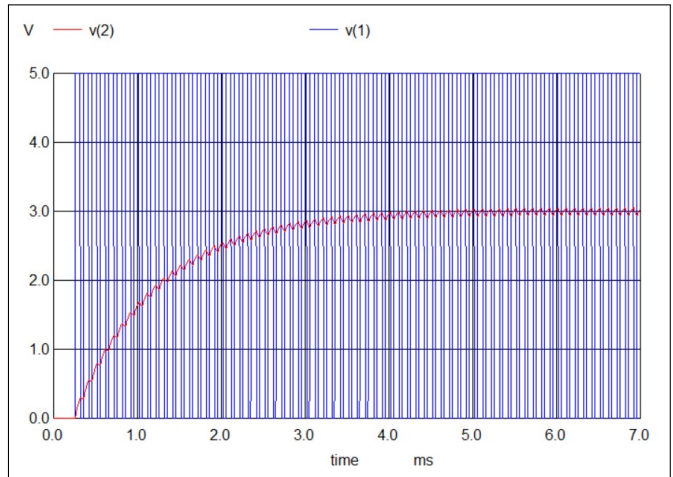



(b) $T = 0.05\tau$

Figure 1: RC Integrator


2 RC Differentiator

PartB2.cir:
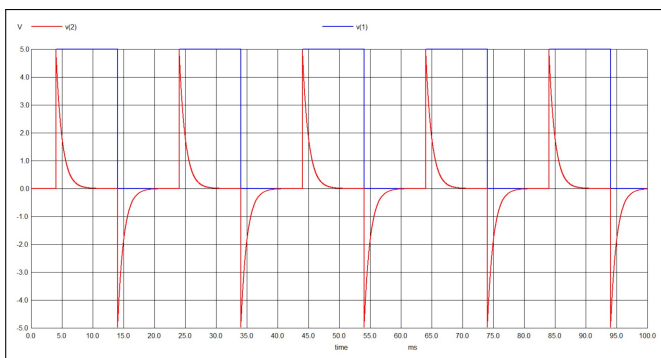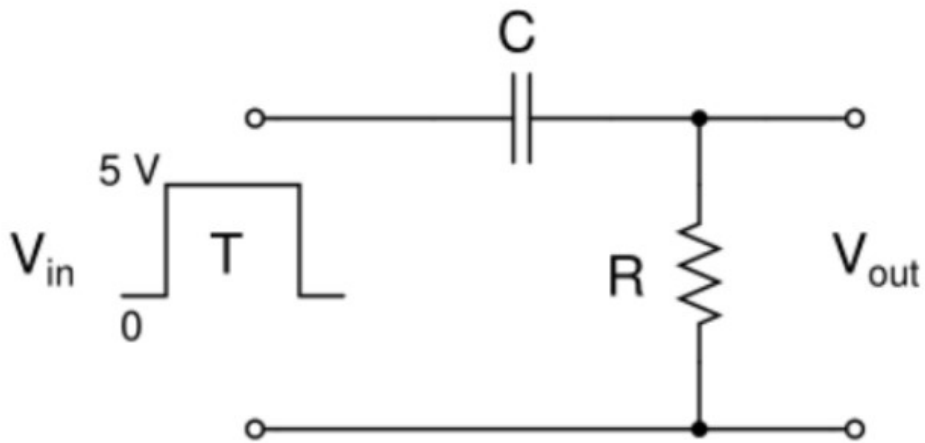
```
1 B2. RC Differentiator Vinamra Baghel 190010070
2 * <element-name> <nodes> <value/model>
3 r 2 0 10k
4 c 1 2 0.1u
5 v 1 0 pulse(0 5 4m 0 0 10m 20m)
6 *analysis command
7 .tran 10u 40m
8 .control
9 run
10 plot v(2) v(1)
11 .endc
12 .end
```



(a) $T = 10\tau$

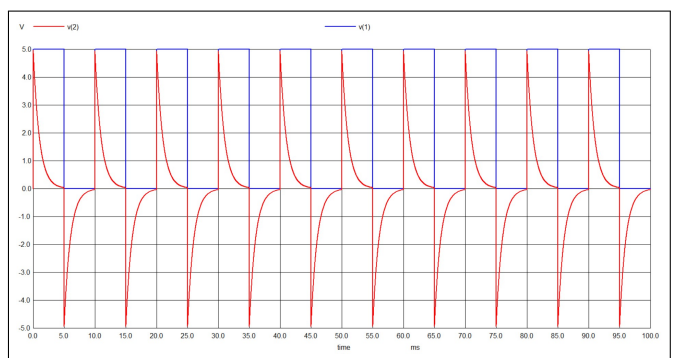



(b) $T = 5\tau$

Figure 2: RC Differentiator


3 RC Lowpass Filter

PartB3.cir:
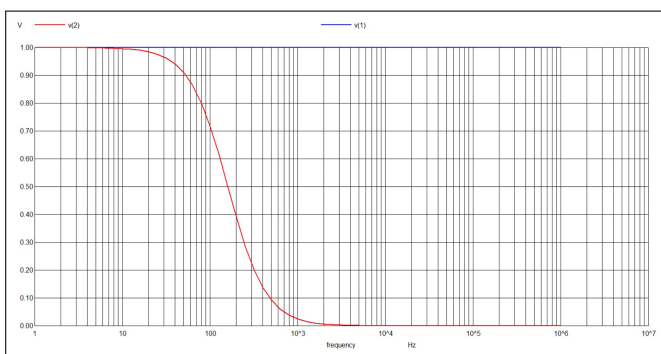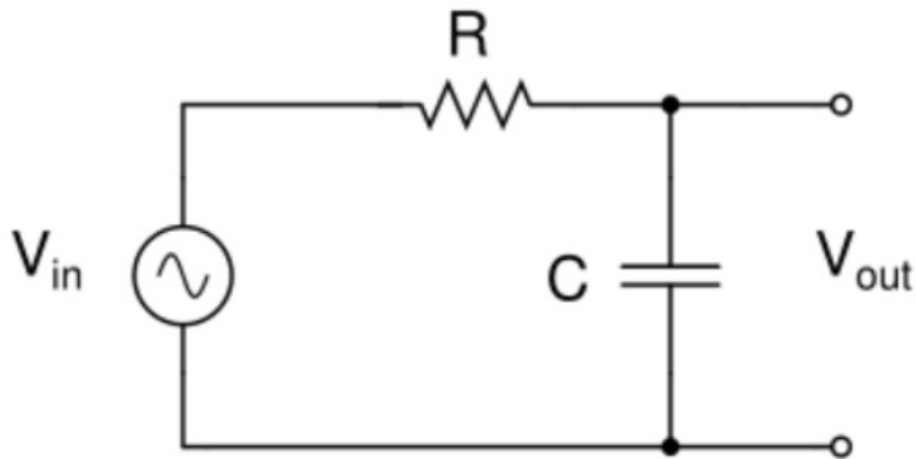
```
1 B3. RC Lowpass Filter Vinamra Baghel 190010070
2 * <element-name> <nodes> <value/model>
3 r 1 2 10k
4 c 2 0 0.1u
5 vin 1 0 dc 0 ac 1
6 *analysis command
7 .ac dec 10 1 1Meg
8 .control
9 run
10 set color0 = white
11 set color1 = black
12 set color2 = red
13 set color3 = blue
14 set xbrushwidth = 2
15 plot vdb(2) vdb(1)
16 .endc
17 .end
```



(a) Linear Scale

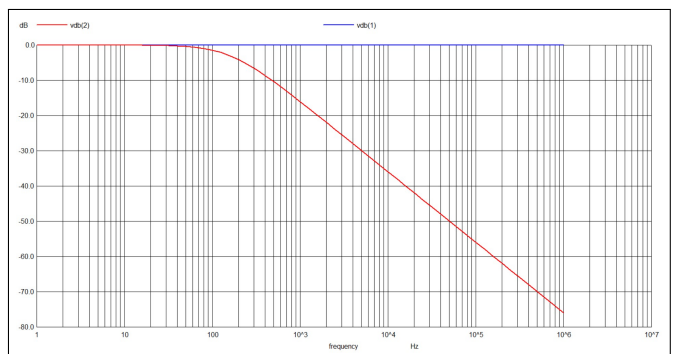



(b) Decibel Scale

Figure 3: RC Lowpass


4 RC Highpass Filter

PartB4.cir:
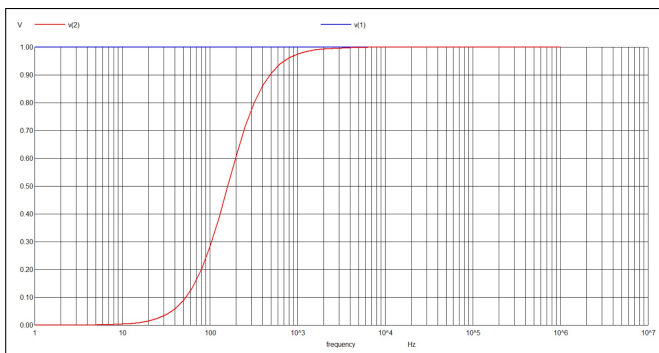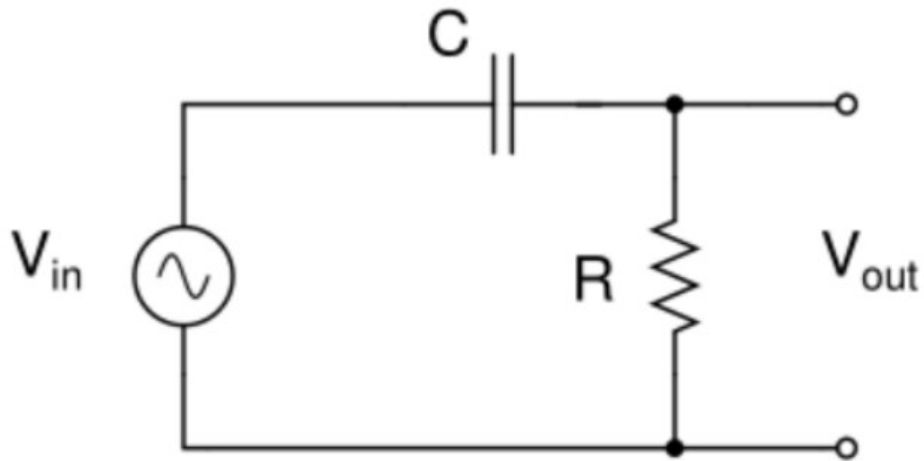
```
1 B4. RC Highpass Filter Vinamra Baghel 190010070
2 * <element-name> <nodes> <value/model>
3 r 2 0 10k
4 c 1 2 0.1u
5 vin 1 0 dc 0 ac 1
6 *analysis command
7 .ac dec 10 1 1Meg
8 .control
9 run
10 set color0 = white
11 set color1 = black
12 set color2 = red
13 set color3 = blue
14 set xbrushwidth = 2
15 plot vdb(2) vdb(1)
16 .endc
17 .end
```



(a) Linear Scale

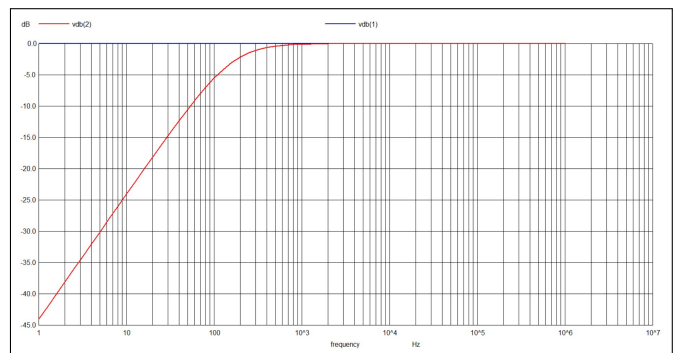

(b) Decibel Scale

Figure 4: RC Highpass


5 RC Bandpass Filter

PartB5.cir:

```

1 B5. RC Bandpass Filter Vinamra Baghel 190010070
2 * <element-name> <nodes> <value/model>
3 r 1 2 10k
4 c 2 3 0.1u
5 r 3 0 10k
6 c 3 0 0.1u
7 vin 1 0 dc 0 ac 1
8 *analysis command
9 .ac dec 10 1 1Meg
10 .control
11 run
12 plot vdb(3) vdb(1)
13 meas ac peak MAX vmag(3)
14 meas ac fpeak WHEN vmag(3) = peak
15 let f3db = peak/sqrt(2)
16 meas ac f1 WHEN vmag(3)=f3db RISE=1
17 meas ac f2 WHEN vmag(3)=f3db FALL=1
18 .endc
19 .end

```

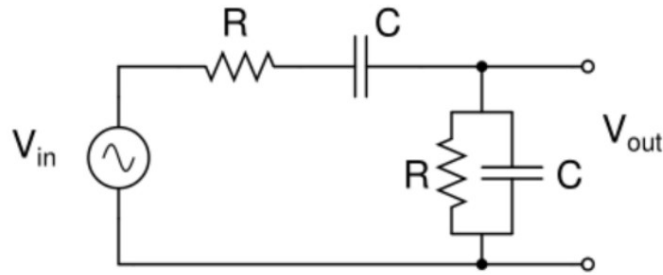


Transfer function = $\frac{1000s}{s^2 + 3000s + 10^6}$. Comparing with $\frac{a_1 s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$,


upper and lower -3dB frequencies: $\omega_1, \omega_2 = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} \pm \frac{\omega_0}{2Q}$, and center-frequency gain = $\frac{a_1 Q}{\omega_0}$

Theoretically: Center frequency, $f_0 = 159.16$ Hz; Lower frequency, $f_L = 47.74$ Hz; and Upper frequency, $f_H = 525.51$ Hz

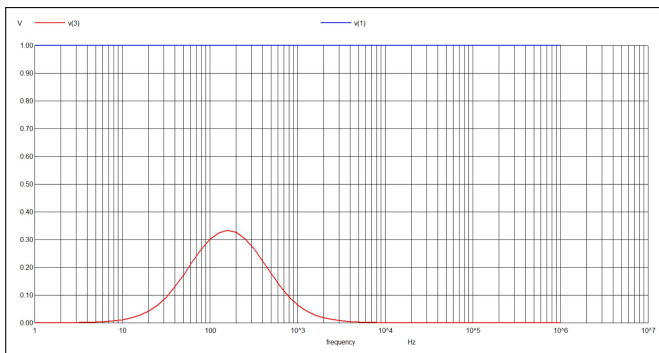From Simulation: Center frequency, $f_0 = 1.584891\text{e}+02$ Hz; Lower frequency, $f_L = 4.838534\text{e}+01$ Hz; and Upper frequency, $f_H = 5.276607\text{e}+02$ Hz



(a) Linear Scale

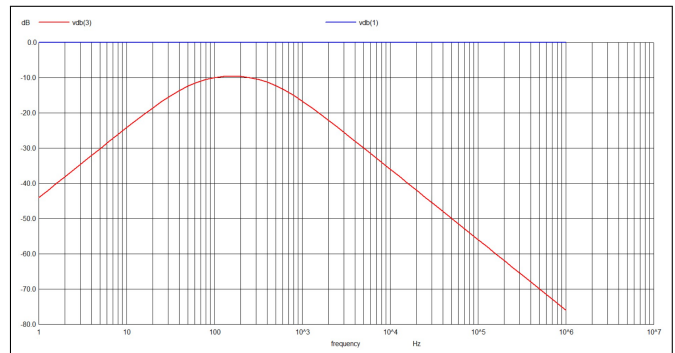

(b) Decibel Scale

Figure 5: RC Bandpass


6 RLC Bandpass Filter

PartB6.cir:

```

1 B6. RLC Bandpass Filter Vinamra Baghel 190010070
2 * <element-name> <nodes> <value/model>
3 l 1 2 10m
4 c 2 3 0.1u
5 r 3 0 1k
6 vin 1 0 dc 0 ac 1
7 *analysis command
8 .ac dec 10 1 10Meg
9 .control
10 run
11 plot vdb(3) vdb(1)
12 meas ac peak MAX vmag(3)
13 meas ac fpeak WHEN vmag(3) = peak
14 let f3db = peak/sqrt(2)
15 meas ac f1 WHEN vmag(3)=f3db RISE=1
16 meas ac f2 WHEN vmag(3)=f3db FALL=1
17 .endc
18 .end

```

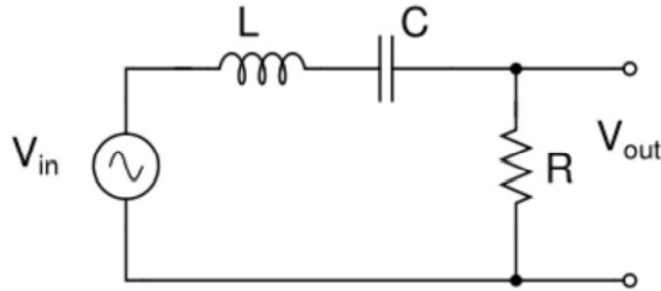


Transfer function = $\frac{1000s}{s^2 + 3000s + 10^6}$. Comparing with $\frac{a_1 s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$,


upper and lower -3dB frequencies: $\omega_1, \omega_2 = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} \pm \frac{\omega_0}{2Q}$, and center-frequency gain = $\frac{a_1 Q}{\omega_0}$

Theoretically: Center frequency, $f_0 = 174605.15$ Hz; Lower frequency, $f_L = 1475.98$ Hz; and Upper frequency, $f_H = 17460.64$ Hz

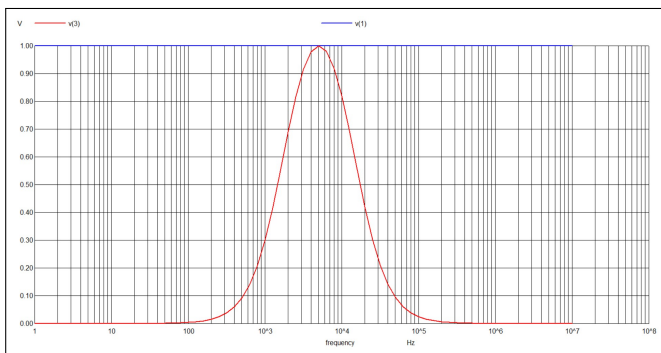From Simulation: Center frequency, $f_0 = 1.74611\text{e}+05$ Hz; Lower frequency, $f_L = 1.468642\text{e}+03$ Hz; and Upper frequency, $f_H = 1.745991\text{e}+04$ Hz



(a) Linear Scale

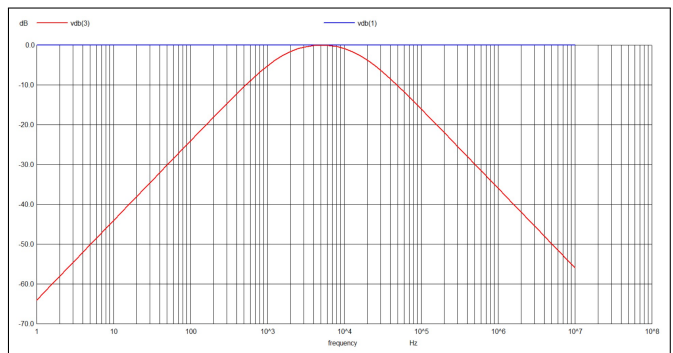

(b) Decibel Scale

Figure 6: RLC Bandpass

Learnings from the experiment

- Circuit simulations using NGSpice Software
- Introduction of Lab Equipments
- XCCircuit Software for Circuit Drawing
- Various RC and RLC Filter Circuits

Challenges faced

- Unfamiliarities with NGSpice Syntax
- Calculation of Center, Upper and Lower -3dB Frequencies

Questions or clarifications: None

Files associated: <https://github.com/VNMR-35/EE-230-Lab>