

# EE 230 Experiment - 8

## Special Opamp Linear Circuits - Precision Rectifiers and Active Filters

1st October, 2021


Vinamra Baghel

190010070


## 1 Precision Rectifiers
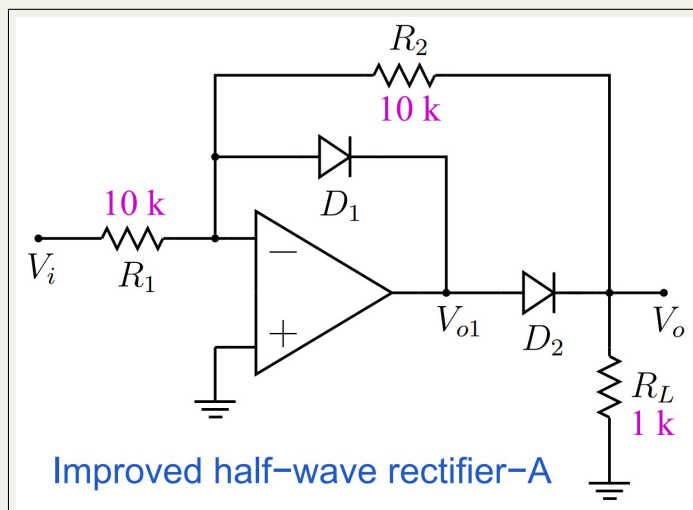
### 1.2 Improved Half Wave Rectifier - A


```
1 Vinamra Baghel 190010070 Improved Half Wave Rectifier-A
2 .include ua741.txt
3 .include IN914.txt
4 *Netlist
5 r1 in neg 10k
6 r2 neg out 10k
7 r1 out gnd 1k
8 D1 neg o1 1N914
9 D2 o1 out 1N914
10 X1 gnd neg pp np o1 ua741
11 Vccp pp gnd 12
12 Vccn np gnd -12
13 Vin in gnd sin(0 1 100 0 0 0)
14 *Analysis
15 .tran 1u 40m
16 .control
17 run
18 plot v(out) vs v(in)
19 .endc
20 .end
```



## Simulation

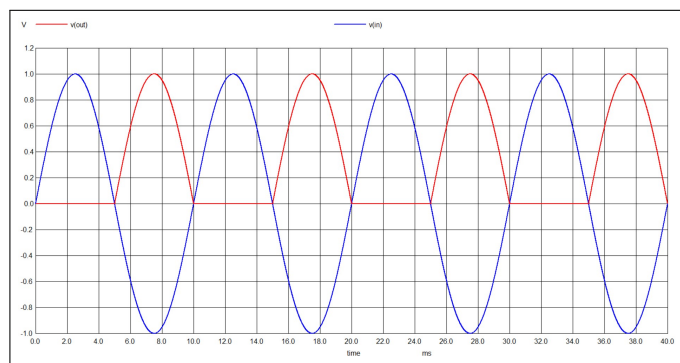

(a)  $V_{in}$  and  $V_{out}$

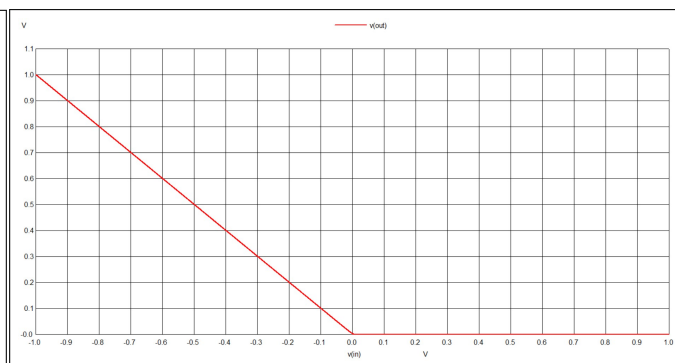

(b)  $V_{out}$  vs  $V_{in}$

## Learnings:

Learnt about the Improved Half-wave rectifier of type A. This rectifier allows the negative part of the input wave pass and outputs it as a positive wave. The model contains diodes  $D_1$  and  $D_2$  which help current pass through the OpAmp in both positive and negative cycles and prevent saturation and delay.

During the positive half-cycle of  $V_i$ ,  $D_1$  is on and  $D_2$  is off; the current flows into the OpAmp;  $V_o$  is 0. During the negative half-cycle of  $V_i$ ,  $D_2$  is on and  $D_1$  is off; the current flows from the OpAmp;  $V_o$  is  $-V_i$ .


We also saw the OpAmp output terminal,  $V_{o1}$  behaves during operation. We can see an offset voltage which is equal to the voltage drop across the diode.

## 1.4 Full Wave Rectifier


```

1 Vinamra Baghel 190010070 Full Wave Rectifier
2 .include ua741.txt
3 .include IN914.txt
4 *Netlist
5 r1 in neg1 10k
6 r2 neg1 in1 10k
7 rs1 in neg2 10k
8 rs2 in1 neg2 5k
9 rf neg2 out 10k
10 r1 out gnd 1k
11 D1 o1 neg1 1N914
12 D2 in1 o1 1N914
13 X1 gnd neg1 pp np o1 ua741
14 X2 gnd neg2 pp np out ua741
15 Vccp pp gnd 12
16 Vccn np gnd -12
17 Vin in gnd sin(0 1 100 0 0 0)
18 *Analysis
19 .tran 1u 40m
20 .control
21 run
22 plot v(out) vs v(in)
23 .endc
24 .end


```

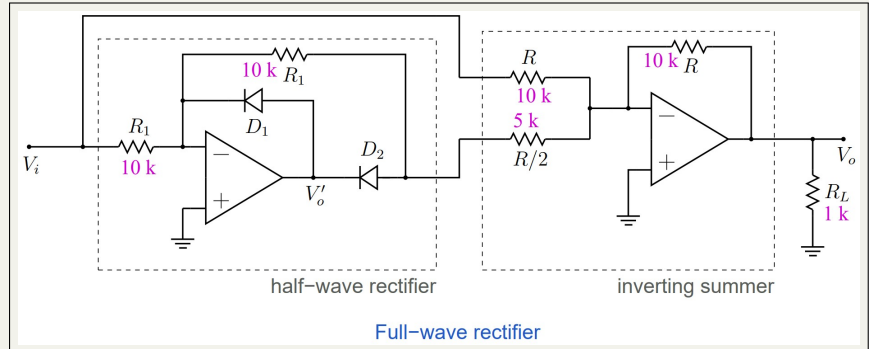

### Simulation

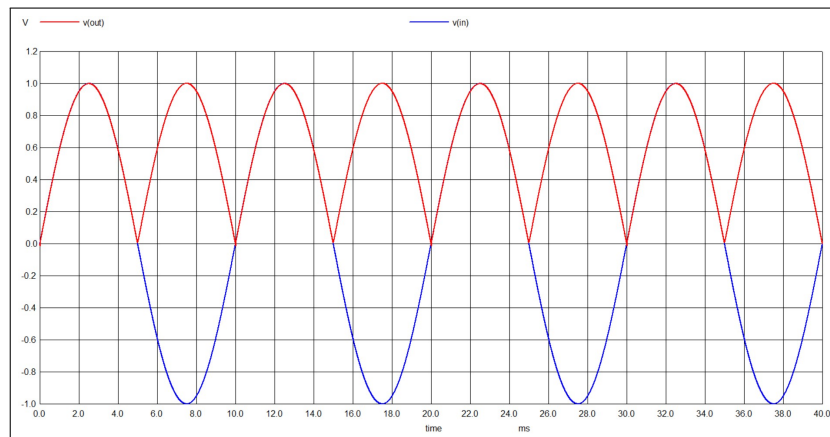

$V_{in}$  and  $V_{out}$

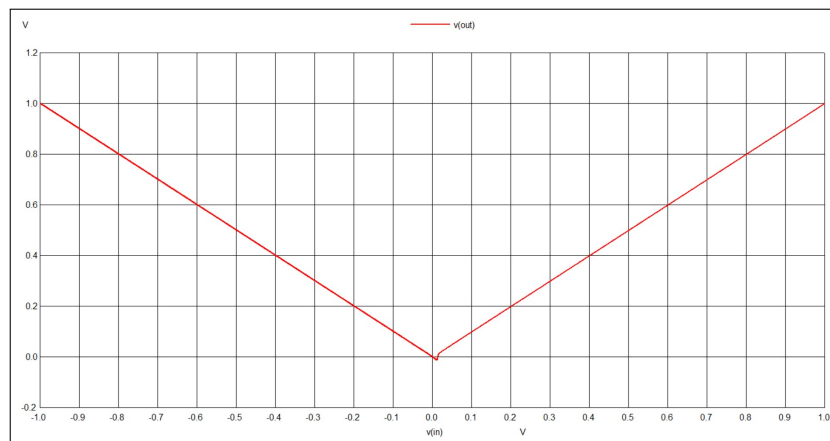

$V_{in}$  vs  $V_{out}$


### Learnings:

Learnt about the Full-wave Rectifier. The full-wave rectifier consists of a Improved half-wave rectifier-B and an inverting summer in cascade. One input of the summer is  $V_i$  and the other is the half-wave rectified wave.

## 2 Active Filters
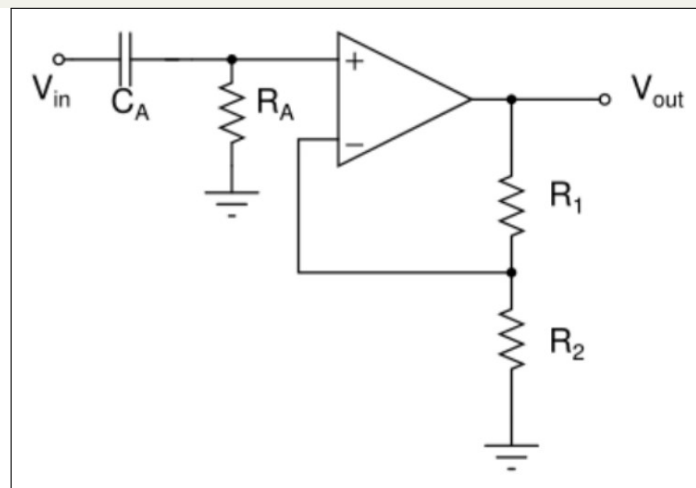
### 2.2 Single-pole Active High-pass Filter


```
1 Vinamra Baghel 190010070 Single-pole Active High-pass Filter
2 .include ua741.txt
3 *Netlist
4 r1 out neg 9.1k
5 r2 neg gnd 1k
6 ra pos gnd 4.7k
7 ca in pos 0.1u
8 X1 pos neg pp np out ua741
9 Vccp pp gnd 12
10 Vccn np gnd -12
11 Vin in gnd dc 0 ac 1
12 *Analysis
13 .ac dec 100 1 10k
14 .control
15 run
16 plot vdb(out)
17 .endc
18 .end
```



Single-pole Active High-pass Filter
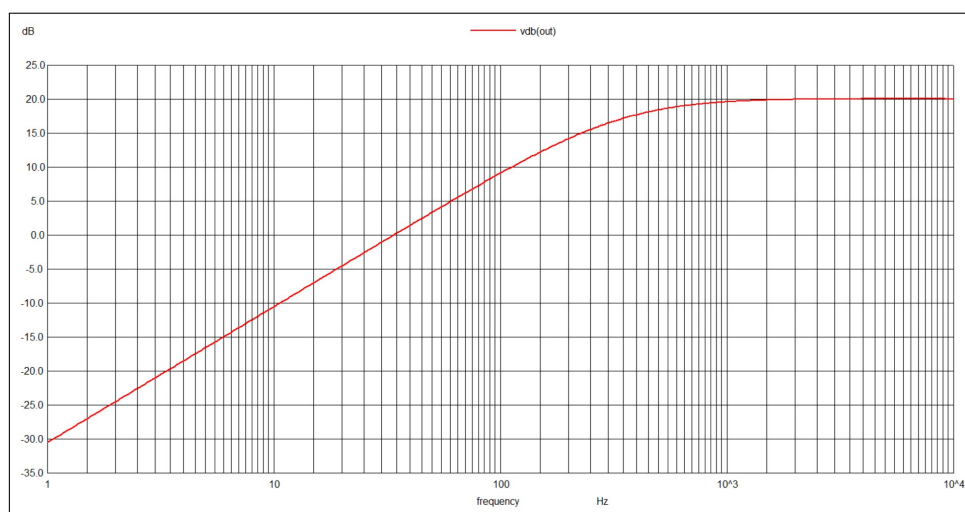
#### Simulation

The cut-off frequency is given by  $f_c = \frac{1}{2\pi R_A C_A} = 338.63 \text{ Hz}$ . The slope of the curve is +20 dB. We can see that both these values check out from the graph.



#### Learnings:

$V_{out}$  in dB


Learnt about the Single-pole Active High-pass Filter. It has many advantages over a passive high-pass filter in terms of flexibility and gain. It is essentially a passive filter cascaded with an OpAmp.

## 2.4 Sallen-Key (2-pole) Active Low-pass Filter

```

1 Vinamra Baghel 190010070 Sallen-Key (2-pole) Active Low-pass Filter
2 .include ua741.txt
3 *Netlist
4 r1 out neg 1.8k
5 r2 neg gnd 3.3k
6 ra in 1 4.7k
7 rb 1 pos 4.7k
8 ca 1 out 0.1u
9 cb pos gnd 0.1u
10 X1 pos neg pp np out ua741
11 Vccp pp gnd 12
12 Vccn np gnd -12
13 Vin in gnd dc 0 ac 1
14 *Analysis
15 .ac dec 100 1 10k
16 .control
17 run
18 plot vdb(out)
19 .endc
20 .end


```

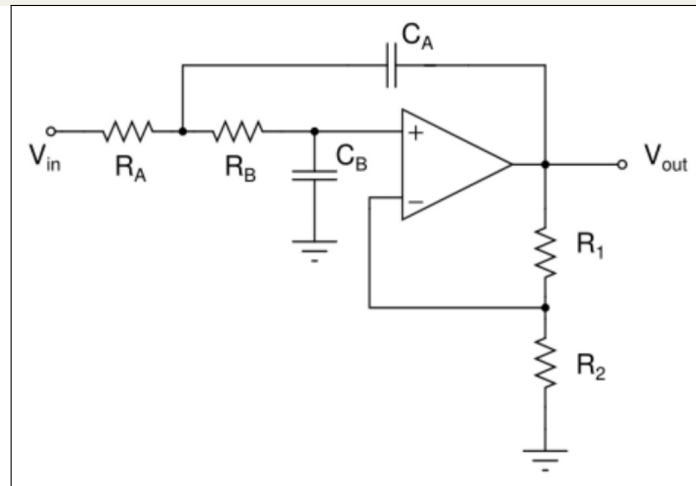

Sallen-Key (2-pole) Active Low-pass Filter
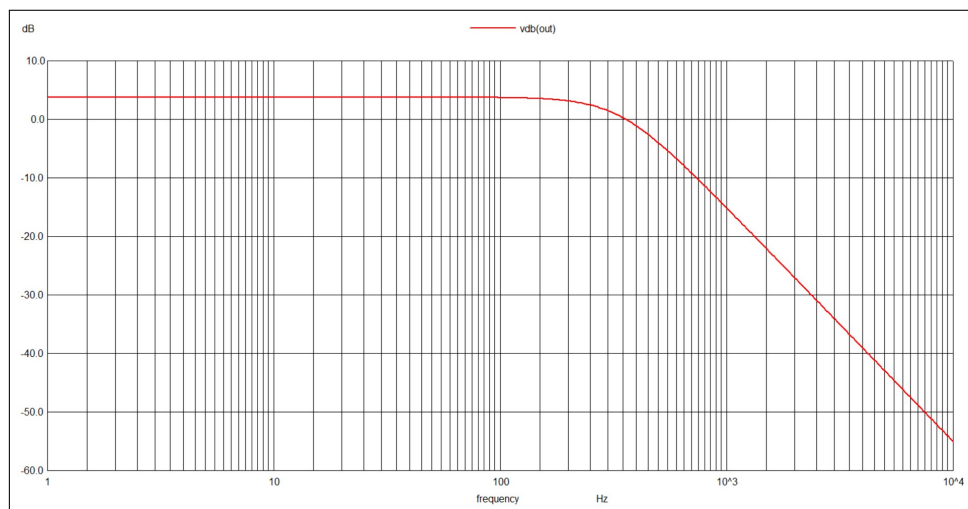
### Simulation

The cut-off frequency is given by  $f_c = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}} = 338.63 \text{ Hz}$ . The slope of the curve is  $-40 \text{ dB}$ . We can see that both these value check out from the graph.



### Learnings:

$V_{out}$  in dB

Learnt about the Sallen-key (2-pole) Active Low-pass Filter. It is essentially a 2-pole passive filter cascaded with an OpAmp. The transfer function obtained is of the order 2.

Files associated: <https://github.com/VNMR-35/EE-230-Lab>